

Differential Amplifier Design and Validation

1. Introduction

Objective:

- Design and validate a differential amplifier, focusing on AC performance, stability, and layout implementation.

Approach:

- Utilized Synopsys Custom Compiler for schematic design, simulation, and layout implementation.

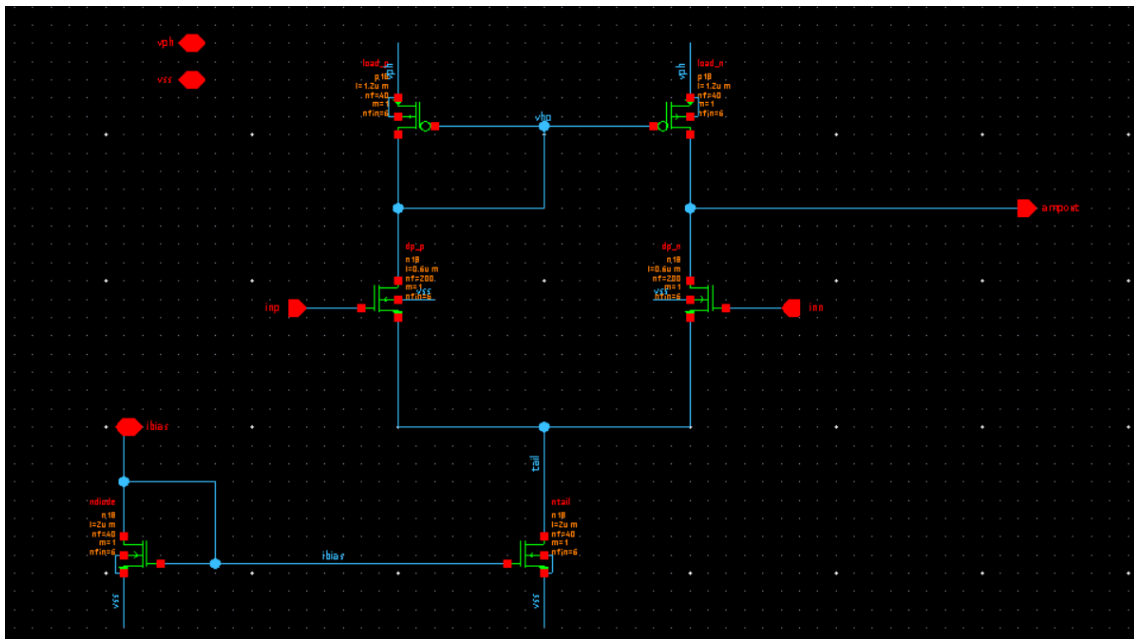


Figure 1 - Circuit of the Differential Amplifier.

2. Methodology

Design Process:

- Followed Synopsys' analog design flow, encompassing schematic creation, AC analysis, and layout verification.

Simulation Setup:

- Conducted simulations for DC gain, bandwidth, stability (LSTB), and PSRR using a 1.8V power supply at typical transistor models and 25°C.

Key Steps:

- Dimensioning:** Replaced the current source with a resistor to achieve $I_{BIAS} = 100\mu A$.
- Validation:** Simulated under various corners (temperature and voltage variations).
- Implementation:** Finalized with layout and design rule checks (DRC).

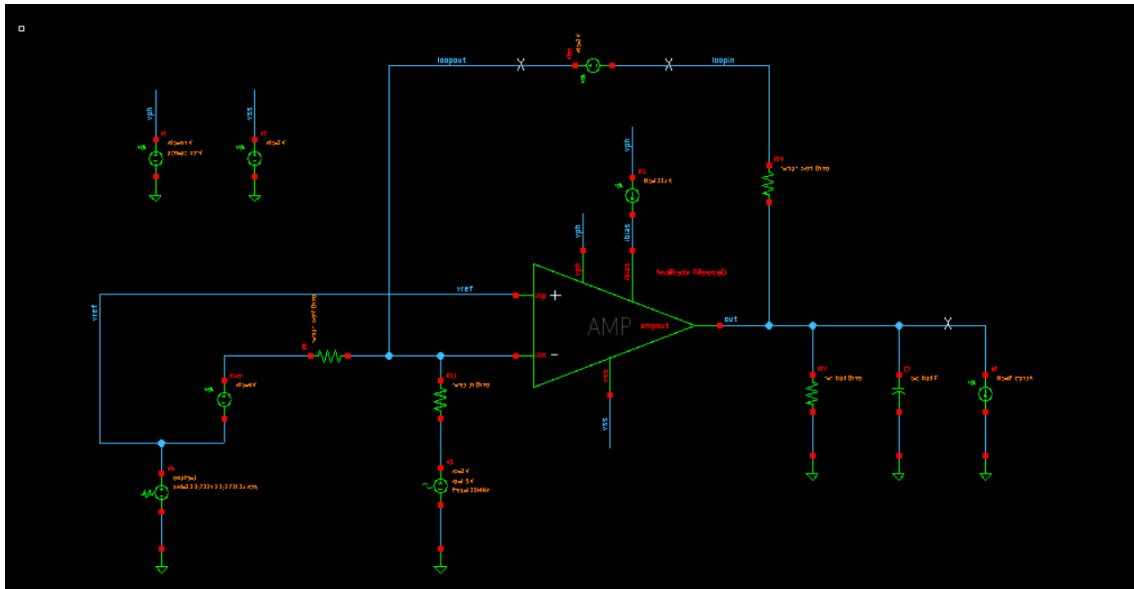


Figure 2 - Testbench Circuit.

3. Results

3.1 AC Analysis

- **DC Gain:** Achieved 51.3 dB.
- **Bandwidth (GBW):** 171MHz.
- **Phase Margin:** 74.88°, indicating stability.

 


Figure 3 - Bode Diagram.

Tabela 1 - Phase Margin Values.

| Phase Margin | Phase Margin Frequency |
|--------------|------------------------|
| 74.8753 | 170.840 MHz |

3.2 PSRR Analysis

- Demonstrated effective suppression of power supply noise, especially at ~400MHz.

 


Figure 4 - PSRR Analysis.

3.3 Validation and Corners

- Evaluated across temperature variations (-40°C to 125°C) and process variations (FF, FS, SF, SS).
- Maintained consistent DC gain and bandwidth across scenarios.

 


Figure 5 - Validation Results Under Multiple Corners.

3.4 Slew Rate and Overshoot

- **Slew Rate:** Achieved $94.8 \text{ V}/\mu\text{s}$, ensuring rapid response to input variations.
- **Overshoot:** Minimal at 3.79 mV , indicating stable performance.

 


Figure 6 - Overshoot Measurement.

 


Figure 7 - Slew Rate Analysis.

3.5 Layout

- Achieved compact design with an area of 750.50 μm^2 .
- Passed DRC with no violations.

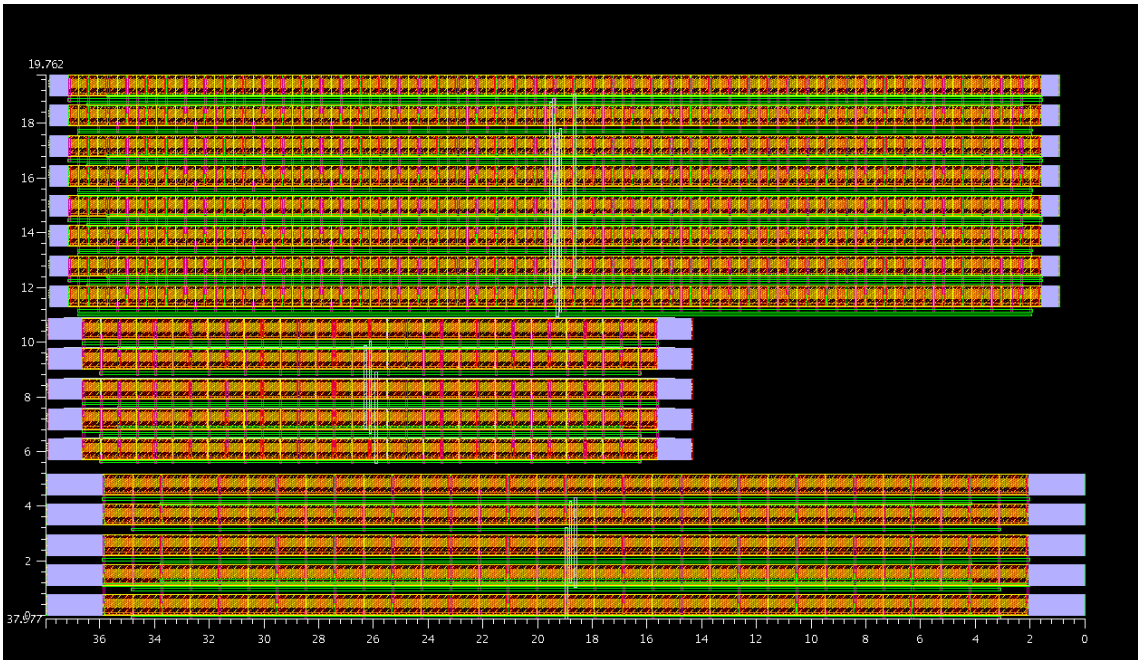


Figure 8 - Layout Representation.

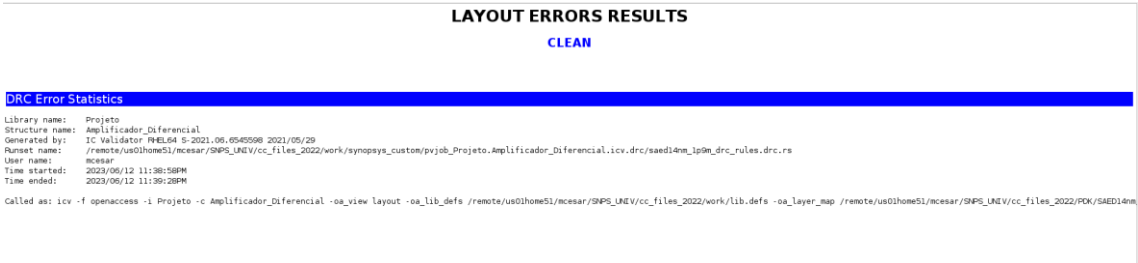


Figure 9 - DRC Verification.

4. Conclusion

Summary:

- Successfully designed and validated a differential amplifier.
- Met target specifications for gain, stability, and noise rejection.