

Class AB CMOS Amplifier Design

1. Introduction

Objective:

- Design and analyze a Class AB CMOS audio amplifier capable of:
 - Driving a 16Ω load with a 1.2V power supply.
 - Achieving $>54\text{dB}$ gain at 20kHz.
 - Maintaining a phase margin $>55^\circ$ for stability.
 - Limiting input noise to $<100\mu\text{Vrms}$ between 20Hz and 40kHz.

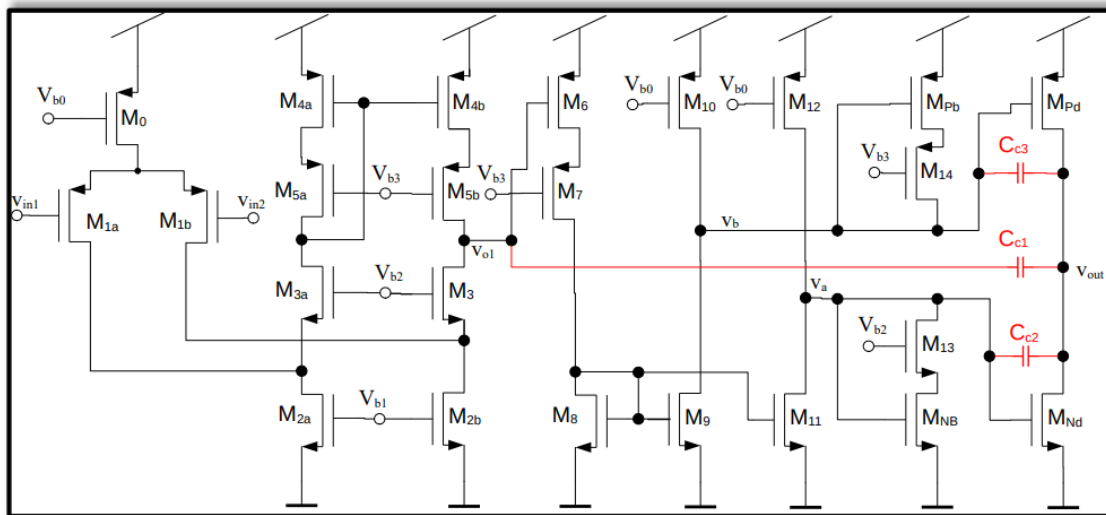


Figure 1 - Class AB Amplifier Circuit.

Approach:

- A combination of circuit modeling, transistor sizing, and simulation was used to meet design specifications while minimizing power consumption and area.

2. Circuit Design and Analysis

- **Circuit Simplification:**

- Nested Miller Compensation was applied to simplify the AC model and facilitate pole-zero analysis.

 


Figure 2 - Simplified Circuit with Nested Miller Compensation.

- **Key Design Parameters:**

- DC Gain: ~59 dB (theoretical), ~28 dB (simulated).
- Dominant Pole (P1): 10 kHz (simulated), 20 kHz (theoretical).
- Phase Margin: Approximately 55°, ensuring stability.
- Noise Performance: Input noise compliant in medium frequencies, with significant flicker noise observed at low frequencies.

3. Methodology

Transistor Sizing:

- Transistors were dimensioned to balance gain, bandwidth, and noise performance:
 - Example M_1 and M_0 ($L_n = 120$ nm, $g_m/I_d = 29.3$).
- Sizing decisions informed by plots of pole and gain behavior.

 


Figure 3 - Pole Frequency Behaviour Plot.

Symbolic Analysis:

- Used Python's SymPy library to derive and validate transfer functions.
- Key equations for poles and zeros simplified for dominant contributions.

4. Simulations and Results

Key Simulation Results:

1. DC Operating Point:

- Verified correct transistor operation, VDSAT values below expected thresholds, indicating potential redesign for optimized operation.

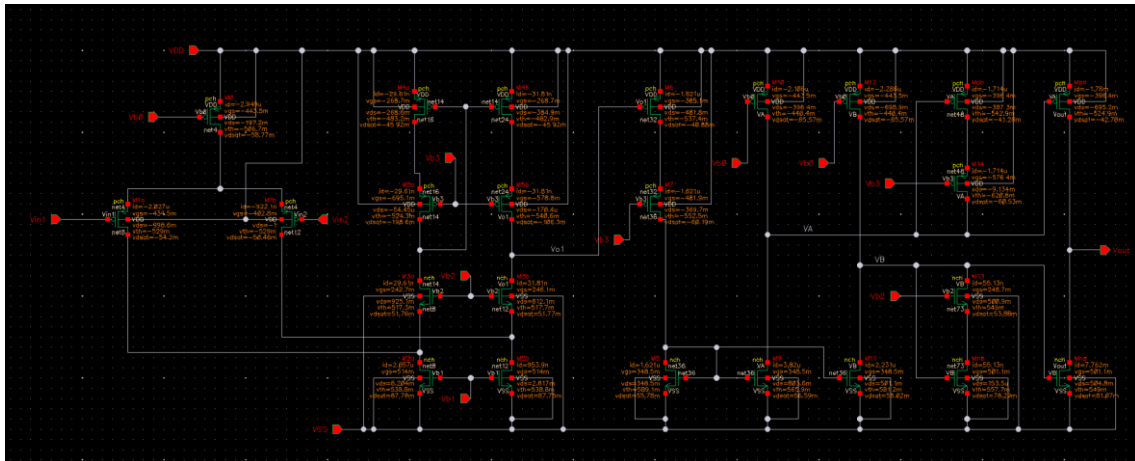


Figure 4 - Operating Point Simulation of the Class AB Amplifier.

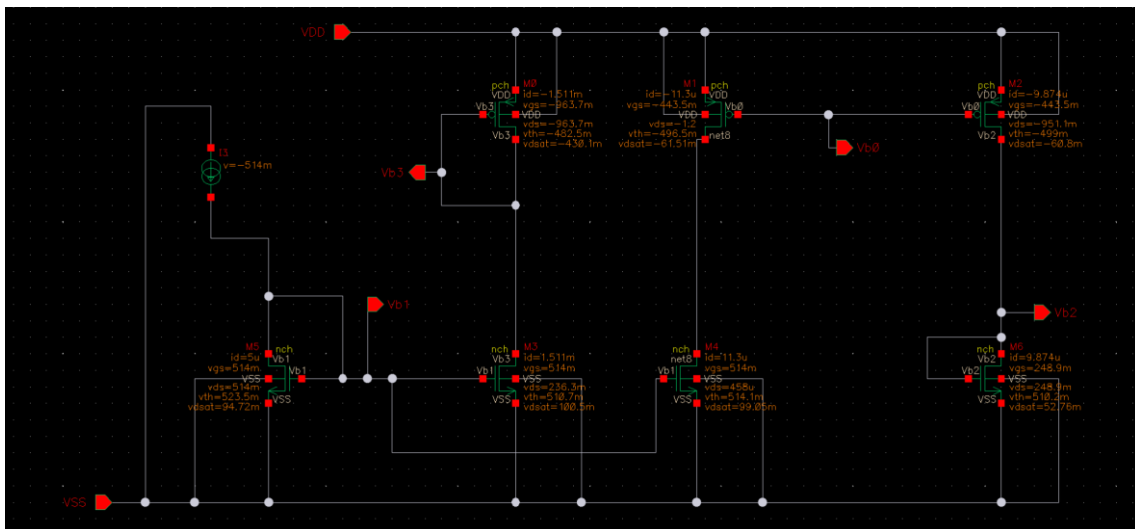


Figure 5 - Operating Point Simulation of the BIAS Circuit.

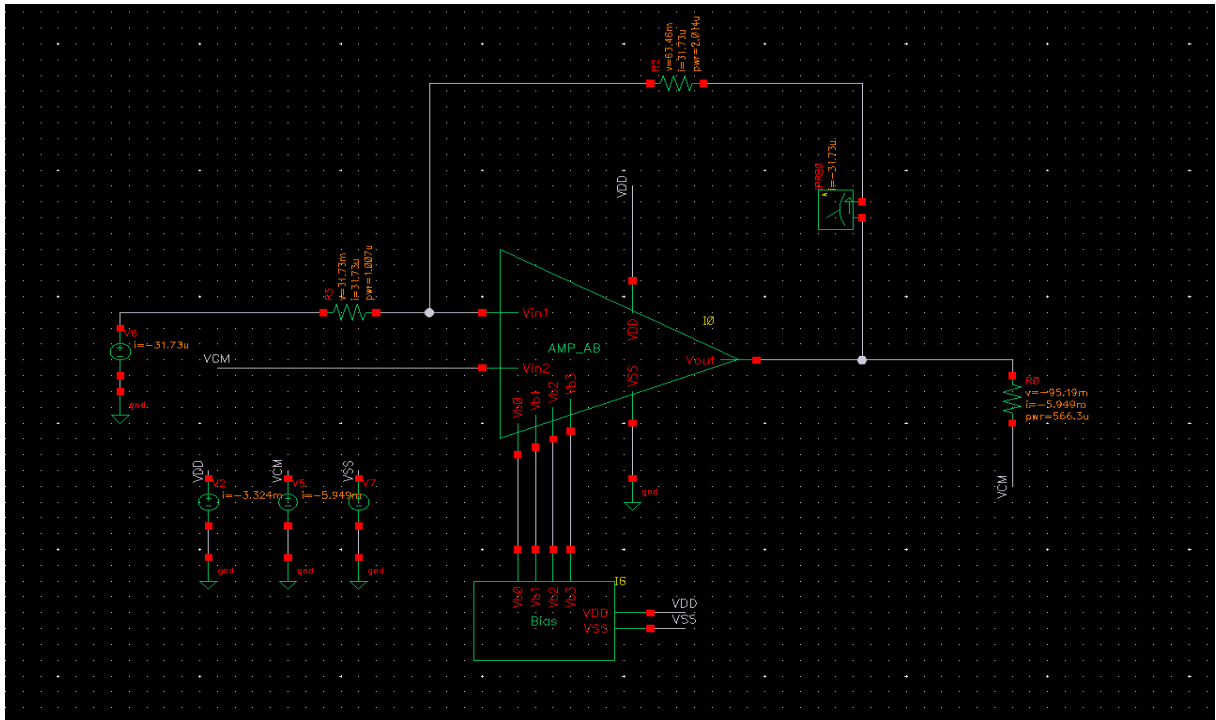


Figure 6 - Operating Point Simulation of the Testbench Circuit.

2. Gain and Phase Stability:

- **Simulated Gain:** ~28 dB.
- **Phase Margin:** Approximately 10°, very distant value from the required specification.

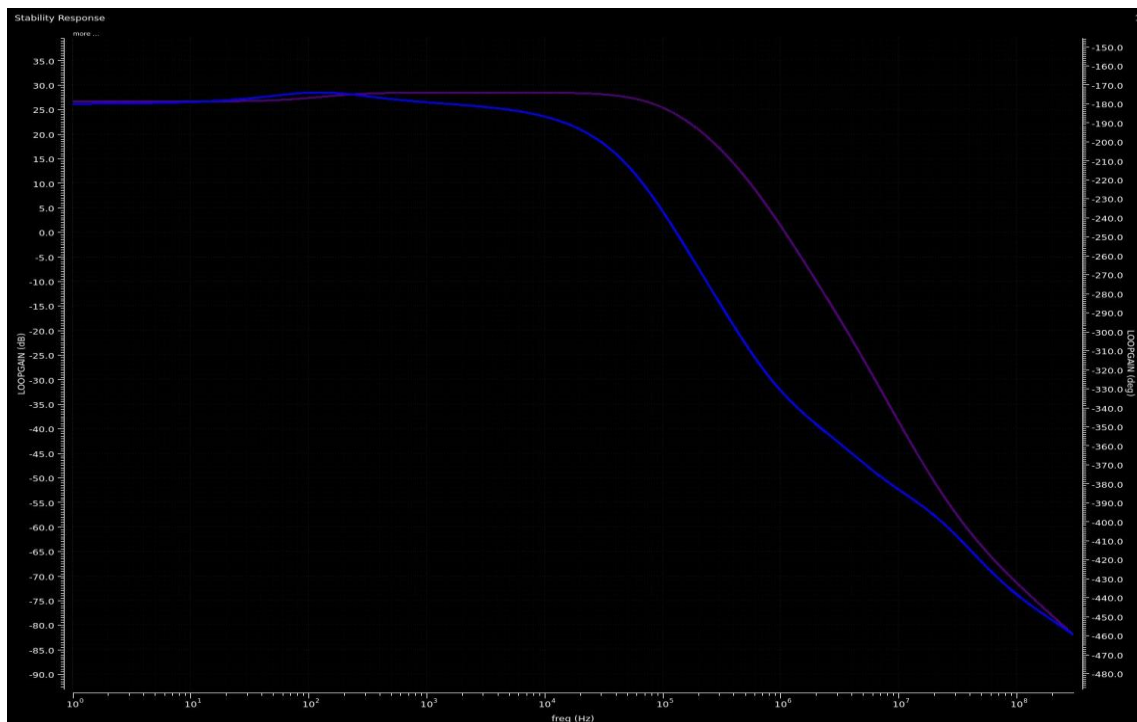


Figure 7 - Closed Loop Simulation Plot.

3. Noise Analysis:

- Input noise within acceptable limits in medium frequencies.
- Flicker noise prominent at low frequencies; suggested mitigation via additional filtering.

 


Figure 8 – Input Referred Noise Simulation Plot.

4. Power Supply Rejection Ratio (PSRR):

- Strong performance at low frequencies; drop-off at higher frequencies.

 


Figure 9 - PSSR Simulation Plot.

5. Time-Domain Analysis:

- Stable output with minimal distortion under a 400mV input signal.

 


Figure 10 - Time Domain Operation Plot of the Closed Loop Circuit.

5. Conclusion

Strengths:

- Stable, low-distortion output for a 400 mV input signal.
- Noise compliance in medium frequencies.

Areas for Improvement:

- **Gain:** ~28 dB(below the required >54 dB).
- **Phase Margin:** ~10° (below the required >55°), indicating instability. Compensation design must be revised.
- **Flicker Noise:** Significant at low frequencies, requiring mitigation strategies.
- **PSRR:** Performance drops at high frequencies and needs optimization.
- **Transistor Sizing:** Biasing conditions and V_{DSAT} should be re-evaluated for improved operation.