

# Folded-Cascode Amplifier Design and Optimization

## 1. Introduction

### Objective:

- Design and simulate a folded-cascode OTA in 130nm CMOS technology, optimizing key performance metrics like DC gain, GBW, and area.

### Motivation:

- Folded-cascode OTAs are essential in high-speed, low-power applications such as switched-capacitor circuits.

### Specifications:

- DC Gain:** >66dB;
- GBW:** >100MHz;
- Second Pole Frequency:** >200MHz;
- Third Pole Frequency:** >1GHz;
- Power Dissipation:** <0.15mW;
- Area:** Minimized for cost-effective design.

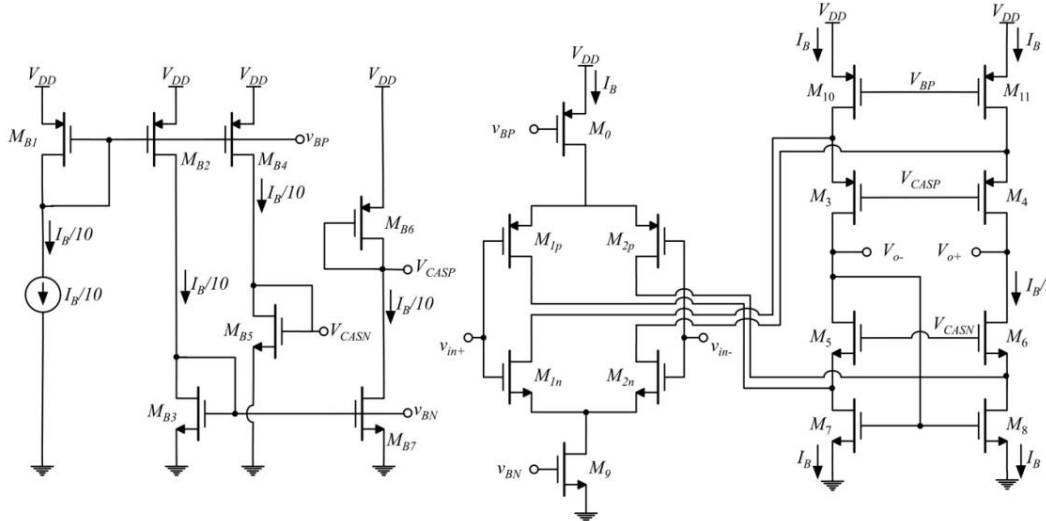


Figure 1 - Schematic of the Folded-Cascode OTA Circuit.

---

## 2. Methodology

### Design Process:

1. Used Mathcad for dimensioning transistors to achieve optimal trade-offs.
2. Simulated the circuit in Cadence Spectre for electrical validation and iterative refinement.
3. Focused on balancing transistor lengths (L) and  $V_{DSAT}$  to meet noise, gain, and bandwidth targets.

### Simulation Setup:

- Conducted simulations for DC operating point, gain, bandwidth, and phase performance.
- Validated noise and power metrics.

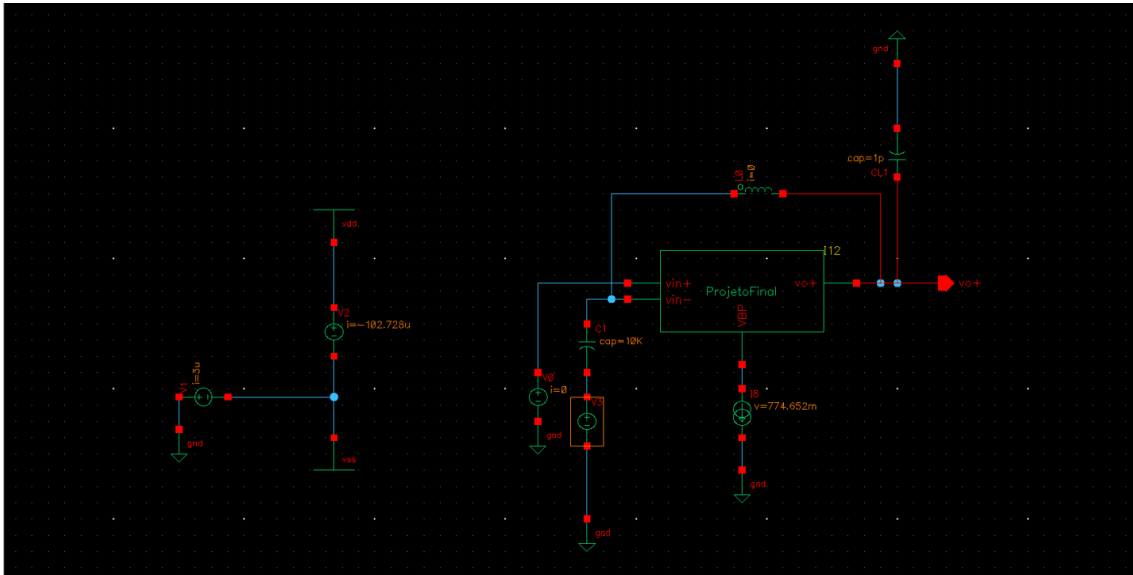


Figure 2 - Cadence Testbench Setup.

### 3. Results

#### 3.1 Key Simulated Metrics

- **DC Gain:** 66.9dB;
- **GBW:** 115MHz;
- **Second Pole Frequency:** 488.2MHz;
- **Third Pole Frequency:** 1.08GHz;
- **Power Dissipation:** 0.12mW;
- **Area:** 187.05 $\mu\text{m}^2$ ;
- **FoM:** 940.2.

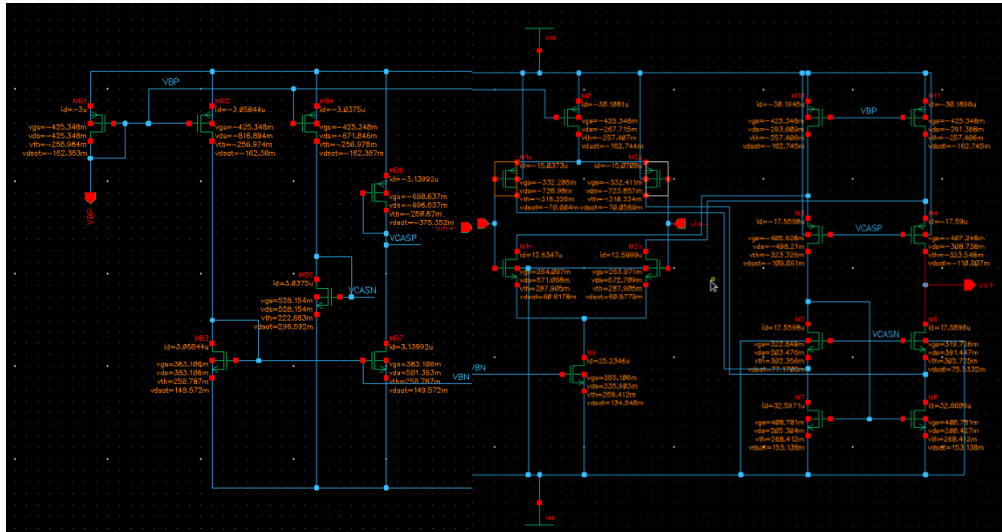


Figure 3 - DC Simulation Results (PFR Analysis).

 


Figure 4 – Simulated Bode Plot.

---

## 4. Discussion

### Key Observations:

- Simulation results closely matched theoretical expectations, validating the design methodology.
- Minor discrepancies in noise and gain were attributed to transistor modeling assumptions.

### Comparison with Previous Designs:

- +4dB improvement in DC Gain compared to prior lab designs.
- +882% improvement in GBW.
- -40% reduction in area.

### Trade-offs:

- Optimizing GBW required adjustments to  $V_{DSAT}$ , affecting power efficiency.

---

## 5. Conclusion

### Summary:

- The project successfully met objectives for DC gain, GBW, and area, showcasing the efficiency of the design approach.
- Demonstrated the importance of iterative optimization in analog circuit design.

### Takeaways:

- Highlights the value of simulation tools like Mathcad and Cadence for achieving real-world performance targets.